

A Trigger Circuit for the 555 Timer IC

Scope

This document describes a trigger circuit that allows the 555 timer IC to produce a voltage pulse when triggered with a voltage that is brought low and held low for an arbitrary amount of time (even longer than the 555 voltage pulse output).

Overview of the Trigger Circuit

The basic monostable 555 timer circuit (see Figure 1) is used to produce an output voltage V_{TIMER} that is a voltage pulse. The output voltage V_{TIMER} is normally low (0V) until the circuit is triggered; after triggering, the output voltage V_{TIMER} transitions from low (0V) to high (5V) for duration $T = R_1 C_1$ (seconds) and then transitions back to 0V. The input voltage V_{TRIG} triggers the circuit; V_{TRIG} is normally held high (5V) and is brought low (0V) momentarily to trigger the circuit.

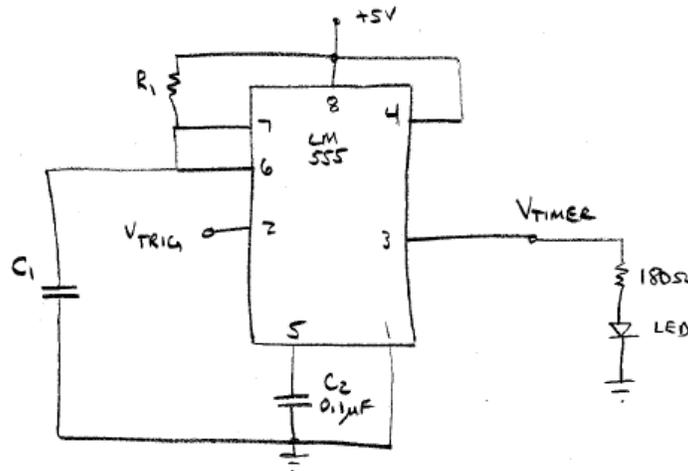


Figure 1. Monostable 555 timer circuit.

V_{TRIG} must be brought low only momentarily; if V_{TRIG} is held low indefinitely, the output voltage V_{TIMER} will remain high indefinitely rather than being a voltage pulse. If it is desirable to trigger the circuit off of the falling edge of a voltage V_{TRIG} that transitions low and remains low indefinitely (while still having a V_{TIMER} pulse duration equal to $T = R_1 C_1$), the trigger circuit in Figure 2 can be used.

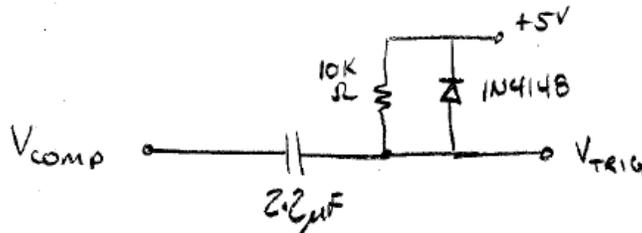


Figure 2. Trigger circuit for the 555 timer IC.

The circuit in Figure 2 produces a momentary low trigger voltage V_{TRIG} on the falling edge of V_{COMP} . V_{COMP} is a voltage that is normally high (+5V) and is brought low (0V) to trigger the 555 timer IC. (The input voltage is named V_{COMP} since it can be the output voltage of a comparator circuit.) When V_{COMP} transitions from +5V to 0V and remains at 0V, V_{TRIG} falls to 0V and then exponentially rises to +5V. This means that V_{COMP} can be brought low and held low, but V_{TRIG} is only momentarily brought low and is suitable for triggering the 555 timer IC. When V_{COMP} transitions from 0V to +5V, V_{TRIG} rises to approximately 5.6V and decays to 5V; the rising transition has no effect on triggering the 555 timer IC. The capacitor and resistor set the time constant of the transients that occur following edges of V_{COMP} .

Simulation of the Trigger Circuit

Figure 3 shows the schematic for an LTSPICE simulation of the trigger circuit. The source V2 produces the voltage V_{COMP} ; the source is specified with a 1K Ω output resistance using resistor RS (this would be the output resistance of the comparator producing V_{COMP}).

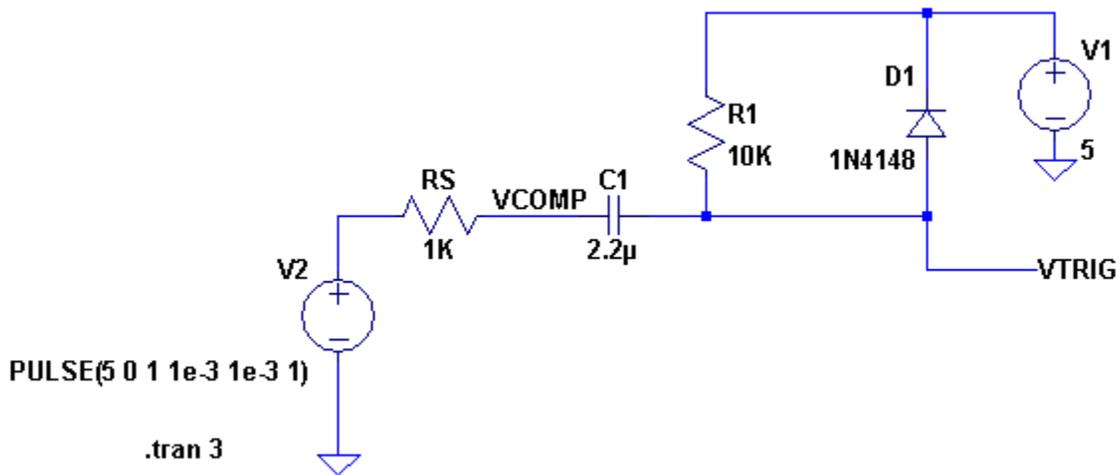


Figure 3. LTSPICE simulation of the trigger circuit.

Figure 4 shows the input voltage V_{COMP} . Figure 5 shows the output voltage V_{TRIG} . When the input voltage V_{COMP} falls from +5V to 0V, V_{TRIG} falls to 0 and rises exponentially with a time constant based on R1 and C1 ($\tau=R_1C_1$). When the input voltage V_{COMP} rises from 0V to +5V, V_{TRIG} shows a voltage spike above +5V. The peak voltage of the spike is limited by diode D1; when V_{TRIG} rises above 5V, diode D1 shunts current and keeps V_{TRIG} from rising significantly above +5V. It has been shown in the lab that this positive spike does not affect triggering of the circuit and does not damage the 555 IC.

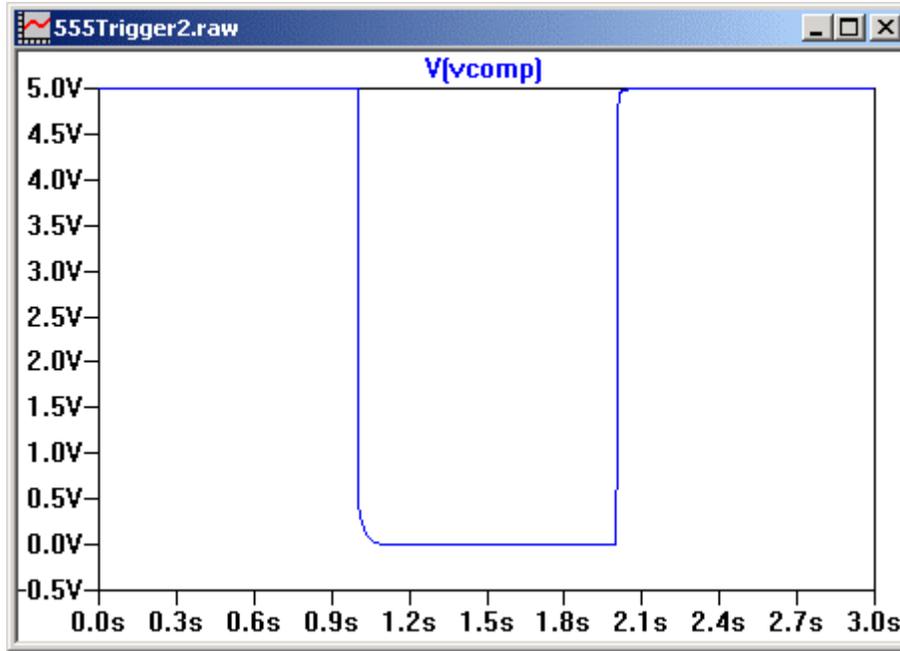


Figure 4. Input voltage VCOMP for the trigger circuit.

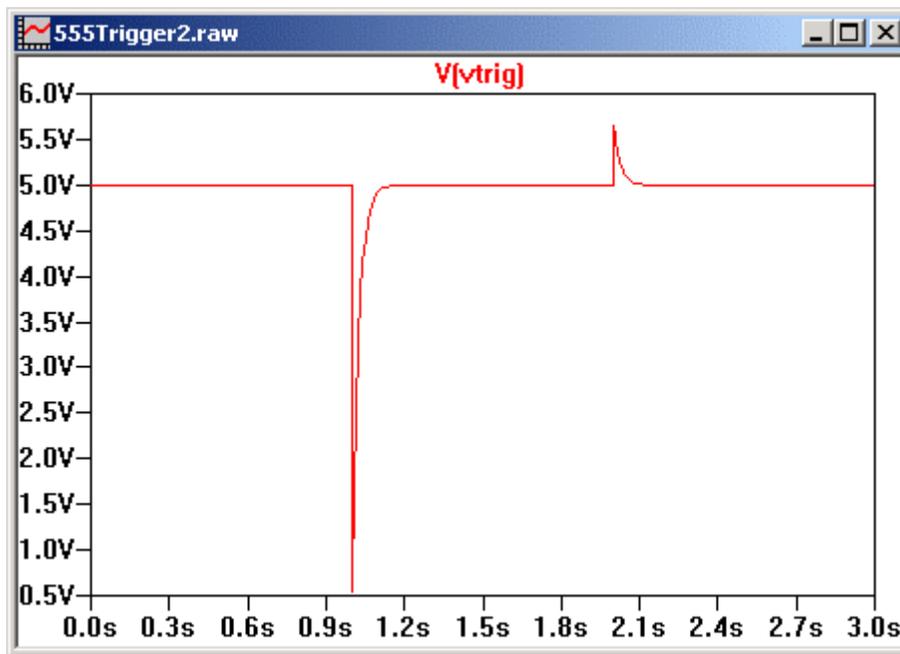


Figure 5. Output voltage VTRIG for the trigger circuit.

Testing the Trigger Circuit

Figure 6 shows a block diagram of the circuit used to test the trigger circuit. The infrared (IR) emitter is an IR light-emitting diode (LED) oriented toward the IR detector. The IR detector is an IR phototransistor oriented toward the IR emitter. The IR emitter and IR detector are separated by a distance of approximately one inch. When nothing obstructs the emitter from the detector, the output voltage of the detector V_{DET} is approximately +4V. The comparator compares V_{DET} to a threshold voltage. When the detector voltage falls below the threshold voltage, the output of the comparator V_{COMP} is approximately 0V (measured to be 0.174V). When the detector voltage rises above the threshold voltage, the output of the comparator V_{COMP} is +5V. The falling edge of the comparator voltage V_{COMP} causes the trigger circuit to trigger the 555 timer as described earlier.


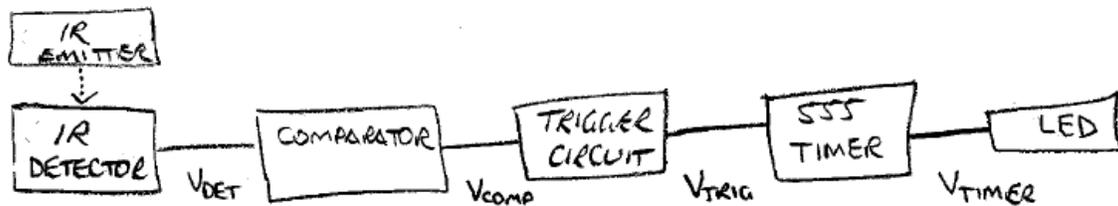


Figure 6. Diagram of test circuit used to test trigger.

Figure 7 shows the schematic of the IR emitter. The resistor was chosen so that approximately 20 mA flow through the IR emitter diode. Figure 8 shows the schematic of the IR detector. The IR detector uses a phototransistor. In the test circuit, the potentiometer connected to the phototransistor's emitter was replaced with a fixed 1K Ω resistor. The output of the detector V_{DET} is 0V when no light is incident upon the detector and +4V when the IR light from the emitter is unobstructed from the detector. The comparator schematic is shown in Figure 9. The potentiometer adjusts the threshold voltage of the comparator. For the test circuit, the threshold voltage was adjusted between 2V and 4V. The output of the comparator is the input to the trigger circuit, and the trigger circuit triggers the 555 timer. The 555 circuit was constructed with $R1 = 560$ K Ω and $C1 = 2.2$ μ F so that the pulse time period was 1.2 seconds. The output of the 555 timer IC was connected to an LED in series with a 180 Ω resistor to indicate the state of the 555 output.

IR EMITTER

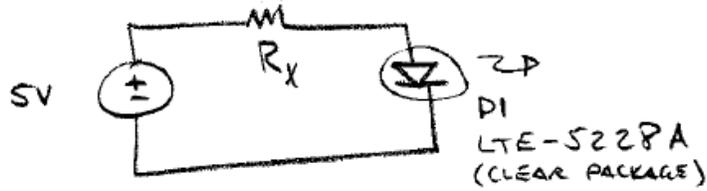FROM DATA SHEET:
 $V_F \approx 1.2V$, $I_F \approx 20mA$



CATHODE HAS NOTCH (SHORT LEAD)

$$R_x = \frac{5 - 1.2}{0.02} = 190 \Omega$$

$$R_1 = 180 \Omega$$

Figure 7. Schematic of IR emitter.

IR DETECTOR

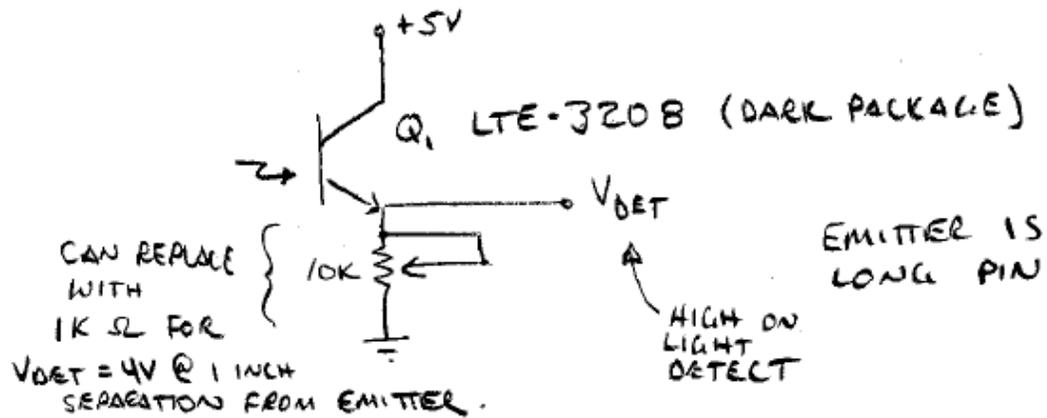


Figure 8. Schematic of IR detector.

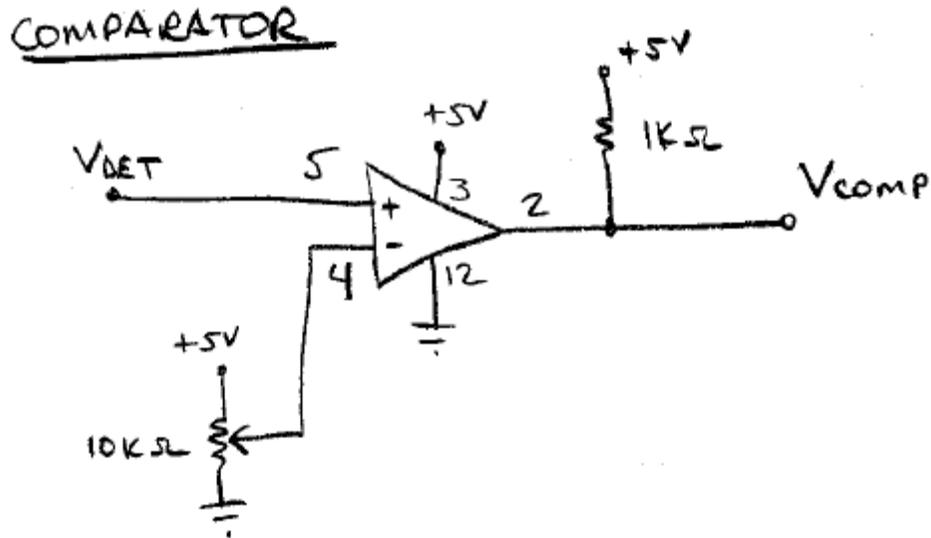


Figure 9. Schematic of comparator.

Figure 10 shows a photo of the test circuit. The IR emitter is on the upper left of the breadboard; the IR detector is on the lower left of the board. The LED on right is normally off and turns on for 1.2 seconds when the light between the IR emitter and IR detector is obstructed. Even if an obstruction is placed between the IR emitter and detector for a long period of time, the LED lights for 1.2 seconds and then turns off.

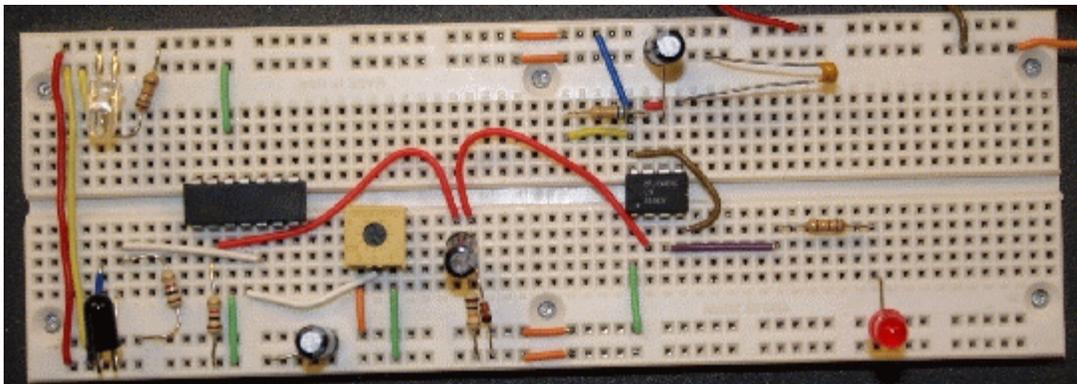


Figure 10. Photograph of the test circuit.

This document is a circuit note for ECEN 3010 lab, University of Colorado at Boulder (William Newhall, 2008).

Source file: Trigger Circuit for 555 (Rev 2008-11-23).doc